

COM 217



File



P. O. Box 845-50400 Busia(K)
principal@auc.ac.ke
Tel: +254 741 217 185
+254 736 044 469
off Busia-Malaba road

OFFICE OF THE DEPUTY PRINCIPAL
ACADEMICS, STUDENT AFFAIRS AND RESEARCH

UNIVERSITY EXAMINATIONS

2018/2019 ACADEMIC YEAR

SECOND YEAR FIRST SEMESTER REGULAR EXAMINATION

FOR THE DEGREE OF BACHELOR OF SCIENCE IN COMPUTER SCIENCE

COURSE CODE: COM 217

COURSE TITLE: ELECTRONICS

DATE: 17TH DECEMBER, 2018

TIME: 2.00 PM – 5.00 PM

INSTRUCTION TO CANDIDATES

- SEE INSIDE

THIS PAPER CONSISTS OF 9 PRINTED PAGES

PLEASE TURN OVER

INSTRUCTIONS TO CANDIDATES

- i. Answer **ALL** Questions from section A and any other **THREE** questions.
- ii. Maps and diagrams should be used whenever they serve to illustrate the answer
- iii. Do not write on the question paper

SECTION A (24 MARKS) COMPULSORY**QUESTION ONE (12 Marks)**

- (a) In the circuit shown in Fig.Q1, determine the values of voltage v_o , and current I_{R1}

(6 marks)

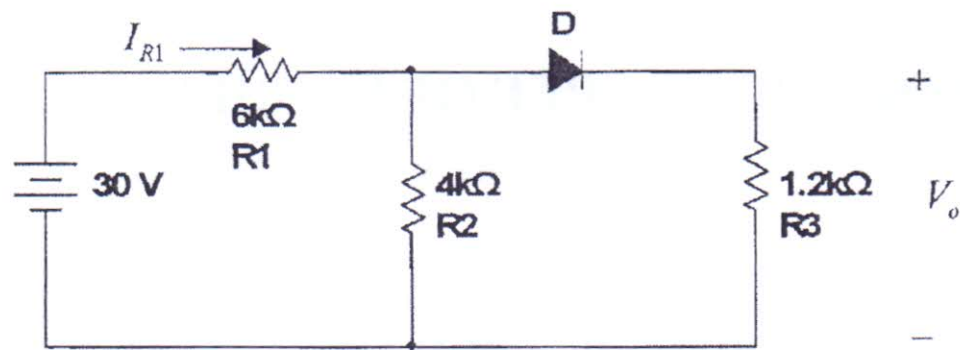


Fig.Q.1a

- (a) The burglar alarm circuit shown in Fig. Q.1b is normally powered from the mains voltage. In the event of a mains power blackout~ a backup battery of 12 V supplies the burglar alarm with power. Explain the role of diodes D 1and D2 in this application. (6 marks)

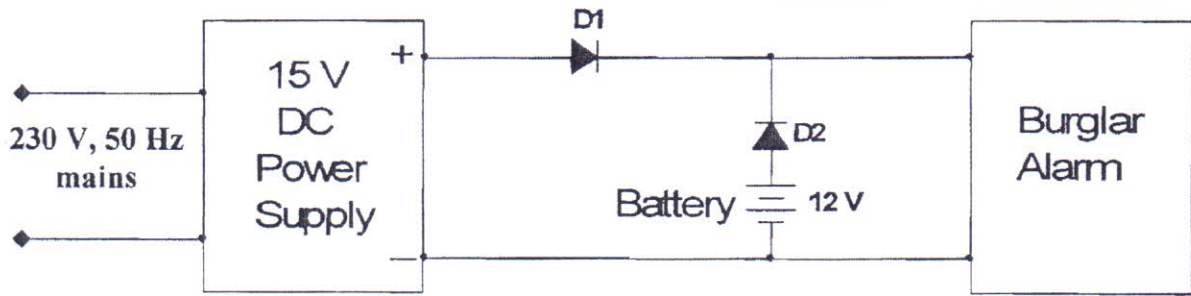


Fig.Q.1b

QUESTION TWO (12 Marks)

For the zener diode circuit shown in Fig.Q.1c:

- Show that the zener diode is operating in the breakdown region. (3 marks)
- Determine the zener diode current. (2 marks)

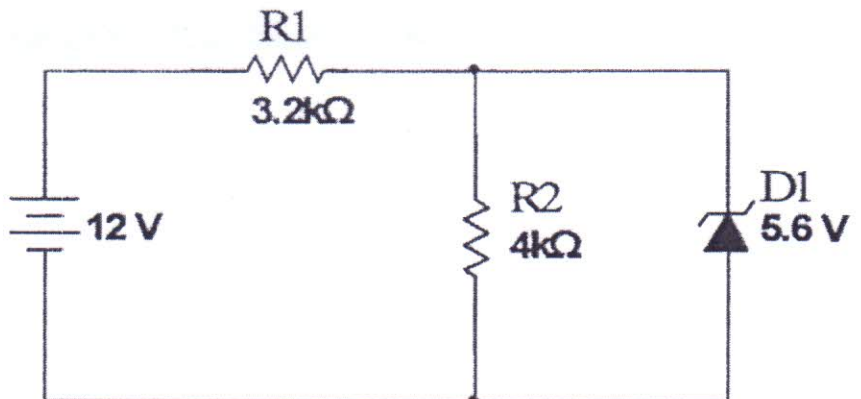


Fig.Q.1c

- If the supply voltage is reduced slowly, determine the voltage at which the zener diode drops out (stops conducting)? (2Marks)
-)

- (d) In the a.c. application of a signal diode shown in Fig. Q.1d determine the voltage ratio v_o/v_{in} . Assume that the capacitors are short circuits at frequencies of interest. (5 marks)

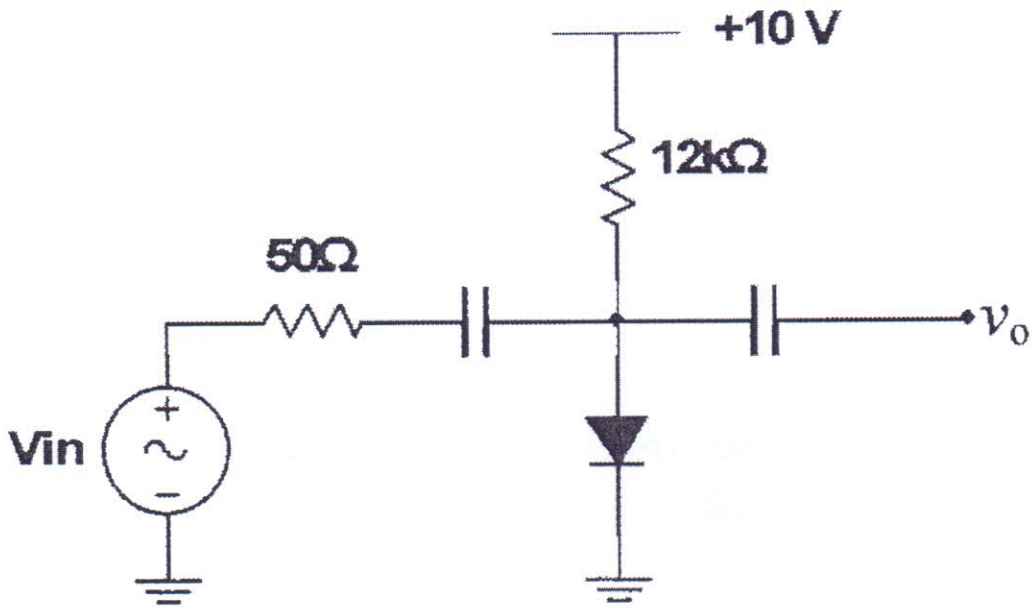


Fig.Q.1d

SECTION B (36 MARKS)

QUESTION THREE (12 Marks)

Determine, stating your arguments, the value of the voltage marked V_L in Fig. Q1.e. Note that the transformer turns ratio is 1 :2. (5 marks)

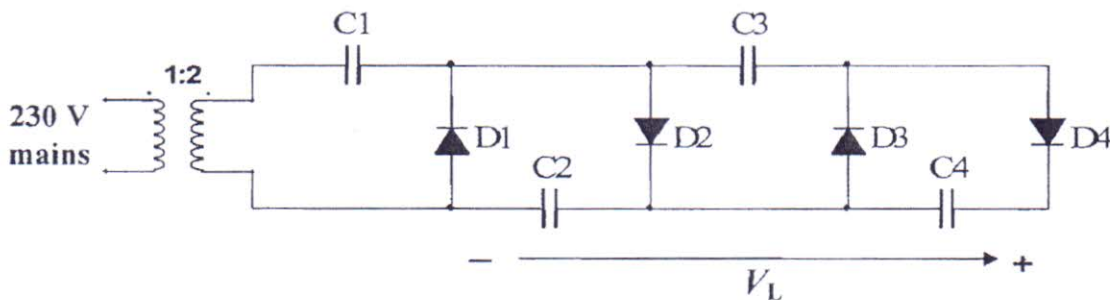


Fig. Q1.e

(f) Design a circuit that lights up all 4 matched light emitting diodes (LEDs). Assume that each the diode has a forward voltage drop of 1.5 V and needs a current of at least 5 mA to light up well. Use a power supply voltage of 5 V. Hint: Decide whether you want series or parallel arrangement. (5 marks)

(g) Design an opamp based function whose inputs and output can implement the function (2 marks)

QUESTION FOUR (12 Marks)

a. Consider the basic transistor circuit shown in Fig. Q.1 h. Assume that the transistor used has $\beta_{dc} = 50$. Determine, giving explanations, the operating mode of the transistor with each of the following component values.

(i) $R_B = 1 \text{ MO}$, $R_C = 5 \text{ k}\Omega$ (6 marks)

(ii) $R_B = 100 \text{ k}\Omega$, $R_C = 10 \text{ k}\Omega$ (6 marks)

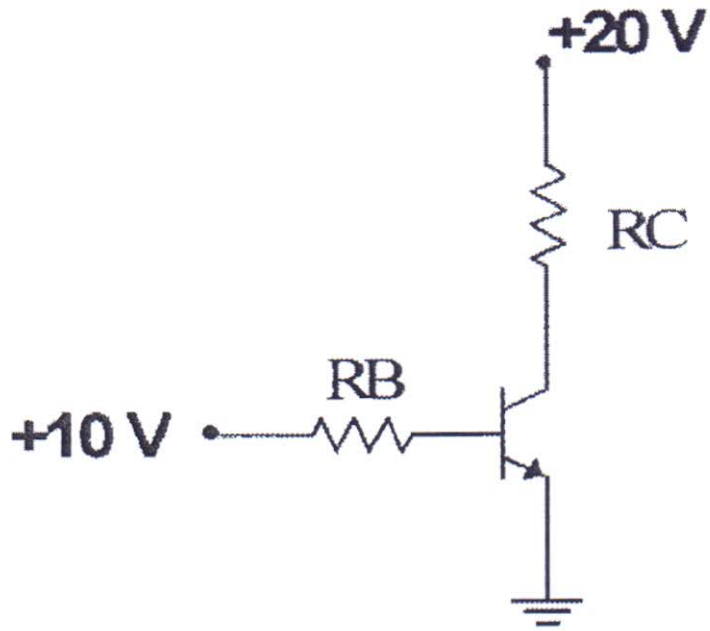


Fig. Q.1h

QUESTION FIVE (12 Marks)

(a) What is the output voltage of the circuit shown in Fig. Q.5a

(4 marks)

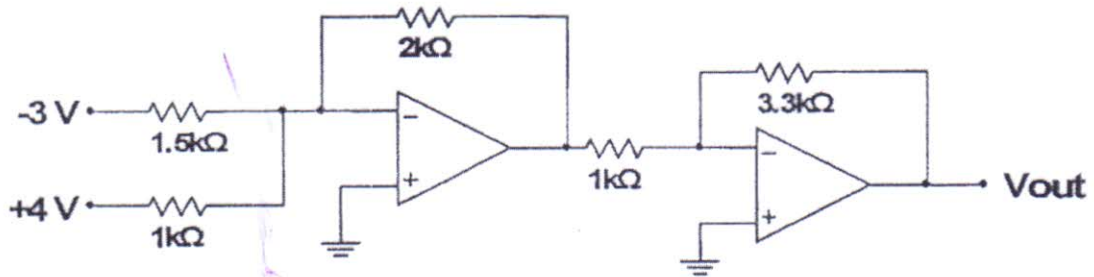


Fig. Q5a

(b) A bipolar 3 V peak-to-peak triangular wave of frequency 109 Hz is applied to the circuit shown in Fig. Q5b. Determine and sketch the output signal of the circuit. (8 Marks)

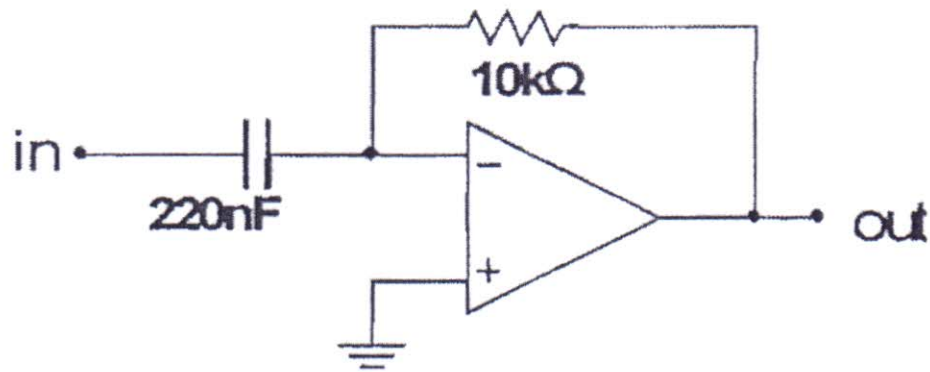


Fig. Q5b

QUESTION SIX (12 Marks)

a) A common emitter npn transistor amplifier works from a 15 V supply. Determine suitable values of R_B , R_C , R_E so that the quiescent operating point is as stable as possible at $I_{CQ} = 10$ mA and $V_{CEQ} \sim V_{CC}/2$ as β varies between 100 and 200.
(6marks)

b) Consider the circuit shown in Fig.Q4. You are given that the transistor used has $\beta = 100$ and $V_A = 75$ V.

- i. Perform d.c. analysis to find the operating point, I_C and V_{CE} , of the transistor. (6marks)
- ii. Assuming that the capacitors used are very large, perform a.c. analysis to find the gain v_o/v_s of the circuit. (6marks)

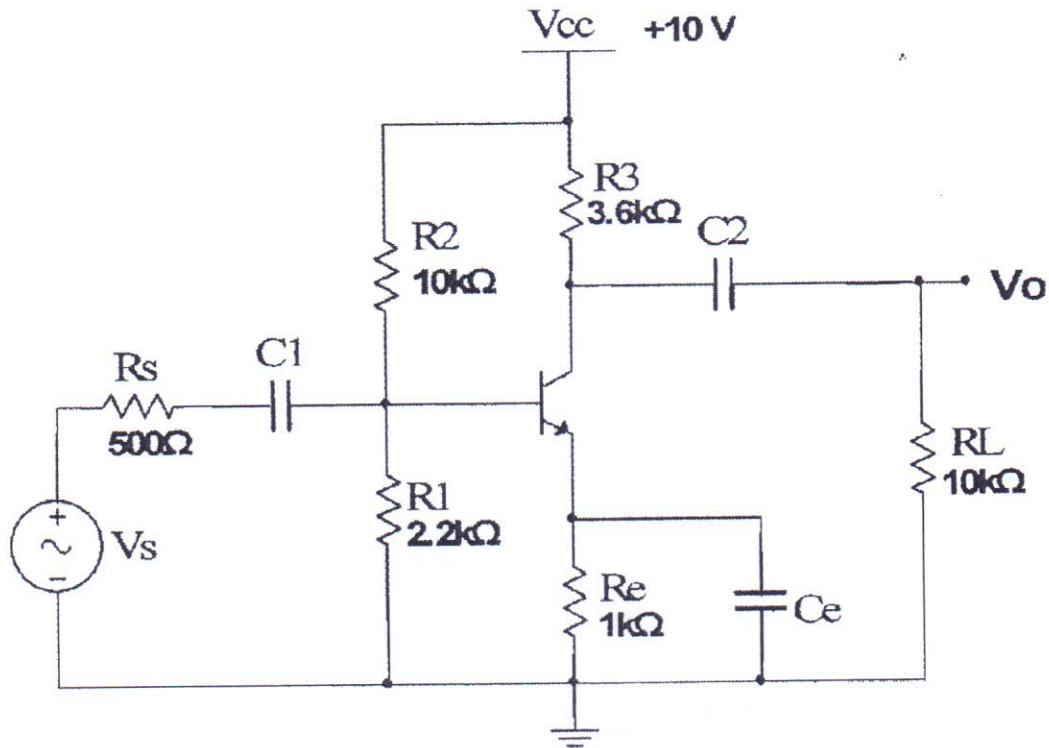


Fig. Q4

QUESTION SEVEN (12 Marks)

A transformer full-wave bridge rectifier is fed from a 230 V, 50 Hz mains supply via a 230V/115V step down transformer. The output of the rectifier is connected to a load resistor R_L of 820Ω in parallel with a smoothing capacitor C of $470 \mu\text{F}$. Assume that the diodes have a voltage drop of 0.7 V when conducting.

Draw the circuit diagram and calculate the following:

- (I) The average d.c. load current.
- (II) The ripple voltage at the load.
- (III) The average d.c. load voltage.
- (IV) The PIV in a diode.
- (V) The peak diode current.

(2 marks)

(2 marks)

(2 marks)

(2 marks)

(2 marks)

(2 marks)

(a) What is the output voltage of the circuit shown in Fig. Q.5a

(4 marks)

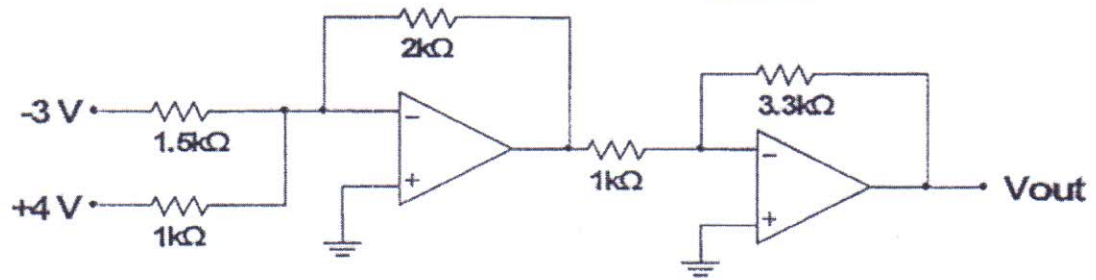
ALUPE UNIVERSITY COLLEGE
LIBRARY

Fig. Q5a